

DR. BABASAHEB AMBEDKAR TECHNOLOGICAL UNIVERSITY, LONERE

Supplementary End Semester Examination – Summer 2022

Course: B. Tech.

Branch: EXTC

Semester : VII

Subject Code & Name: BTETPE703C (VLSI Design & Technology)

Max Marks: 60

Date:22/08/2022

Duration: 3.45 Hr.

Instructions to the Students:

1. All the questions are compulsory.
2. The level of question/expected answer as per OBE or the Course Outcome (CO) on which the question is based is mentioned in () in front of the question.
3. Use of non-programmable scientific calculators is allowed.
4. Assume suitable data wherever necessary and mention it clearly.

(Level/CO) Marks

Q. 1 Solve Any Two of the following.

- A) Implement following Boolean function using PROM, PLA and PAL.

6

$$A(X,Y,Z)=\sum m(5,6,7)$$

$$B(X,Y,Z)=\sum m(3,5,6,7)$$

- B) What is interconnect in SoC?

6

- C) What is JTAG based boundary scan testing?

6

Q.2 Solve Any Two of the following.

- A) Explain CMOS common Gate amplifier.

6

- B) Write VHDL code for 4x1 mux using Concurrent and sequential statements.

6

- C) Explain LUT used in FPGA architecture?

6

Q. 3 Solve Any Two of the following.

- A) Difference between CPLD and FPGA.

6

- B) What is the need of DFT in VLSI?

6

- C) Draw and explain DC transfer characteristics of CMOS inverter.

6

Q.4 Solve Any One of the following.

- A) What are the different types of architectures used in the VHDL? Explain with Half adder as an example.

12

- B) Draw Layout diagram of NAND gate with all dimensions.

12

Q. 5 Solve Any Two of the following.

- A) Draw the CMOS AND and NOR gate.

6

What is the technological reason for using universal gate for design?

- B) What is the difference between Signal and Variable in VHDL

6

- C) Explain Small signal equivalent analysis of MOS Differential Amplifier.

6

***** End *****